

# Lecture 13:

## Digital Logic Cont..

# Announcements



- Project 3 due on Monday
  - Due August 11<sup>th</sup> 11:55pm
  - Due day before Final, so plan accordingly
  - No Extension
- Project 2 grades will be out tonight
- Final Next Wednesday
  - 3 hour timed exam
  - Open for 24-hours
  - Few Sample Questions w/o answers by this weekend
- Lectures until final:
  - Digital Logic (Chapter 4 in book)
  - Today: Adders/ Sequential Circuits
- Rest of lecture time / recitation today:
  - Questions on today's material and programming Assignment 3

# Another Optimization Approach: Karnaugh Maps


- K-maps are a graphical technique to view minterms and how they relate.
- Extremely useful to simplify boolean functions.
- The “map” is a diagram made up of squares, with each square representing a single minterm.
- Minterms resulting in a “1” are marked as “1”, all others are marked “0”
  
# Finding Commonality

- Its usefulness come from the fact that adjacent squares correspond to minterms that differ in only ONE variable.
- Combining  $2^n$  squares eliminate n variables.





# Finding the “best” solution

 


- Grouping become simplified products.
- Both are “correct”. “ $A+B$ ” is preferred.

# Simplify Example

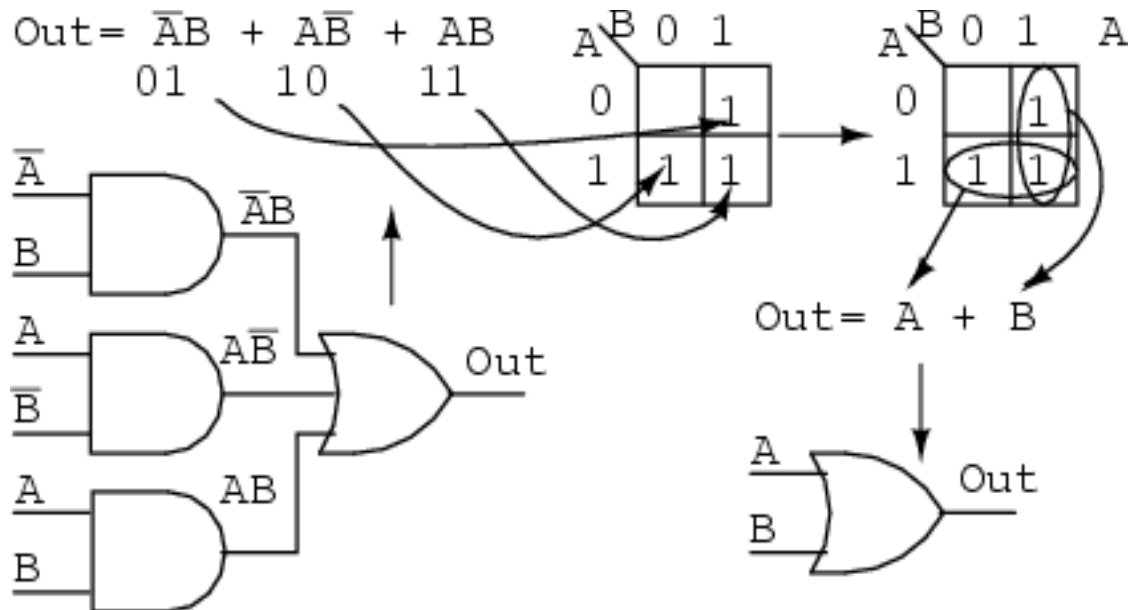 

# 3 Variable K-Maps

 

- Note in higher maps, several variables occupy a given axis
- The sequence of 1s and 0s follow a **Gray Code Sequence**.
- Grey code is a number system where two successive values differ only by 1-bit

# 3 Variable K-Maps (Example 4)

	$\overline{B}\overline{C}$	$\overline{B}C$	$BC$	$B\overline{C}$
$\overline{A}$				
$A$				

$A \backslash BC$	00	01	11	10
0				
1				

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC + AB\overline{C}$$

$A \backslash BC$	00	01	11	10
0	1	1	1	1
1			1	1

$$\text{Out} = \overline{A} + B$$

- Its usefulness come from the fact that adjacent squares correspond to minterms that differ in only ONE variable.
- **Combining  $2^n$  squares eliminate  $n$  variables.**



# 3 Variable K-Maps (Example 5)


	$\overline{B}\overline{C}$	$\overline{B}C$	$BC$	$B\overline{C}$
$\overline{A}$				
$A$				

	$00$	$01$	$11$	$10$
$A$				
$0$				
$1$				

$$\text{Out} = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + \overline{A}B\overline{C} + AB\overline{C}$$

	$00$	$01$	$11$	$10$
$A$				
$0$	1			1
$1$	1			1

$$\text{Out} = \overline{C}$$

 

# Up... up... and let's keep going

		D			
		00	01	11	10
A B	00				
	01				
	11				
	10				


Diagram illustrating a 4x4 Karnaugh map grid. The vertical axis is labeled A/B (00, 01, 11, 10) and the horizontal axis is labeled CD (00, 01, 11, 10). Blue brackets group the columns under 'D', the rows under 'A', and the columns under 'C'. A bracket on the right side groups the columns under 'B'.

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$


		CD			
		00	01	11	10
A B	00	1			1
	01				
	11				
	10	1			1

Diagram illustrating a 4x4 Karnaugh map grid with 1s in the corners. Red dashed lines connect the 1s in the corners, indicating a group of four.

 
$$\text{Out} = \overline{B}\overline{D}$$



# Few more examples

 
 
$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + ABCD$$



$$\text{Out} = \overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{D} + ABCD$$

# Don't Care Conditions

- Let  $F = AB + \bar{A}\bar{B}$
- Suppose we know that a disallowed input combo is  $A=1, B=0$
- Can we replace  $F$  with a simpler function  $G$  whose output matches for all inputs we do care about?
- Let  $H$  be the function with Don't-care conditions for obsolete inputs

Inputs will  
not occur

A	B	F	H	G
0	0	1	1	1
0	1	0	0	0
1	0	0	X	1
1	1	1	1	1

$$G = AB + \bar{B}$$

- Both  $F$  &  $G$  are appropriate functions for  $H$
- $G$  can substitute for  $F$  for valid input combinations

# Don't Cares can Greatly Simplify Circuits

$X=0$

CD \ AB	00	01	11	10
00				
01	1	1	X	1
11			X	X
10	1	1	X	X

$$f = \overline{A}\overline{C}D + \overline{B}\overline{C}D + \overline{A}C\overline{D}$$


$X=1$

CD \ AB	00	01	11	10
00				
01	1	1	X	1
11			X	X
10	1	1	X	X



$$f = \overline{C}D + C\overline{D}$$
 
# Converting Circuits to all-NAND (NOR)

- Introduce NOT gates
  - Go from left to right
  - Introduce NOT gates in pairs (does not alter logic function)
  - Isolated NOT gates can be implemented as NAND (NOR)



# Example

  

Each "o" by itself represents a NOT gate

# Put it all together.....

sensor  
inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\bar{A}BC = 1$$


$$A\bar{B}C = 1$$

$$AB\bar{C} = 1$$

$$ABC = 1$$


$$\text{Output} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

 1. Express the truth table function in SOP (this example) or POS
2. Simplify the function using K-maps (this example) or boolean algebra






# Put it all together.....

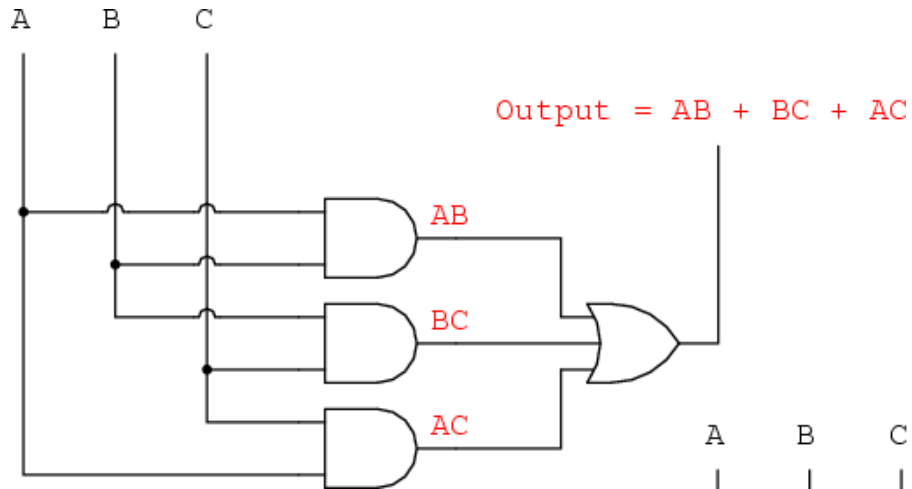

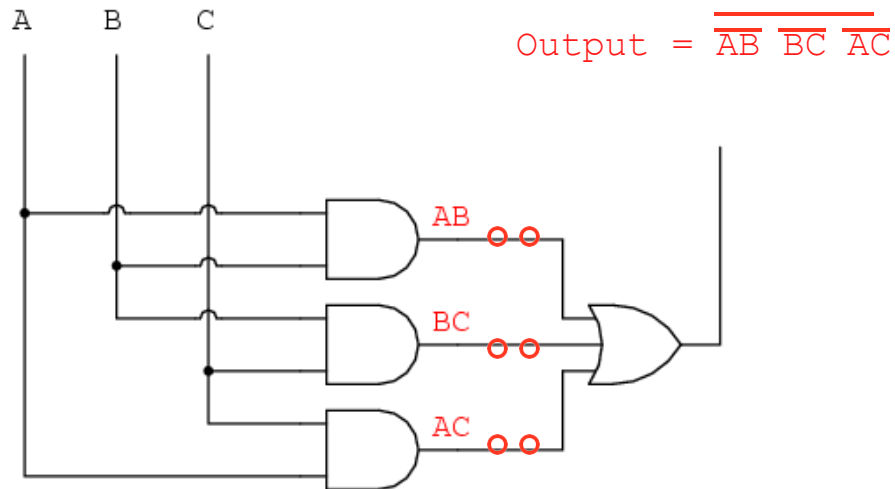3. Convert function to use NAND or NOR gates




# Addition: The Half Adder

Addition of 2 bits: A & B produces summand (S) and carry (C)

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B$$

$$C = AB$$

 

But to do addition, we need 3 bits at a time (to account for carries)

$$\begin{array}{r} 011 \leftarrow \text{carry bits} \\ + 1011 \\ \underline{1001} \\ 10101 \end{array}$$

# The Full Adder

Takes as input 2 digits (A&B) and previous carry (P)

P	A	B	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S:

		B	
0	1	0	1
P	1	0	1
		A	


XOR:checker-board pattern

$$S = A \oplus B \oplus P$$

$$C = AB + AP + BP$$


C:

		B	
0	0	1	0
P	0	1	1
		A	

 
 
# 5-bit Ripple Carry Adder

Computes  $a_4a_3a_2a_1a_0 + b_4b_3b_2b_1b_0$




Note how computation ripples from left to right

- Each adder has depth 2 (input passes through 2 gates to reach output)
- Full adder that computes  $s_i$  cannot start its computation until previous full adder computes carry
- The longest depth in a  $k$ -bit ripple carry adder is  $2k$
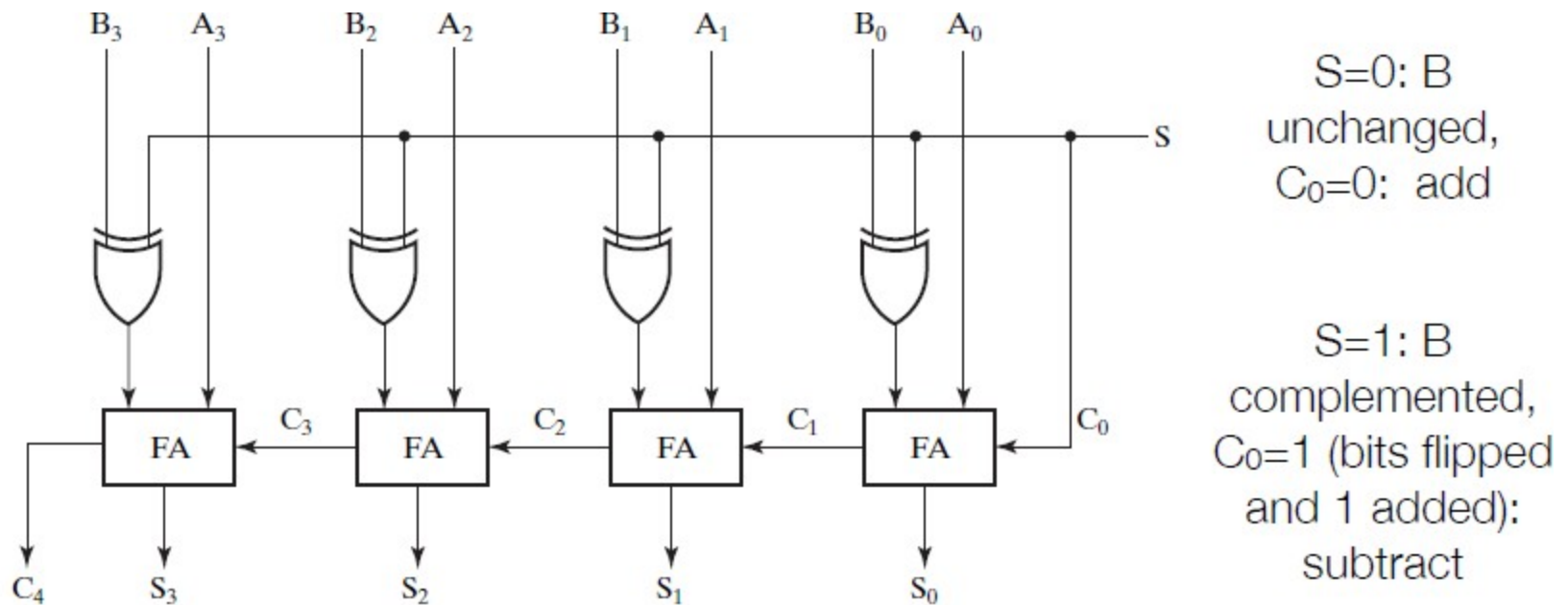
# Adder-Subtractor circuit

How to change the adder to add and subtract using same circuit?

- Add extra bit  $S$  to switch between addition and subtraction
- Add XOR gate at the second input to full-adder



- Addition:  $A + B$
- Subtraction:  $A - B = A + (\text{complement of } B + 1)$

# Handling 2's Complement Overflow

Adding 2 positive numbers ➡➡negative result

$$\begin{array}{r} \phantom{0000}1 \\ \phantom{00}6 \phantom{0000}0110 \\ + \phantom{00}5 \phantom{0000}0101 \\ \hline -5 \phantom{0000}1011 \end{array}$$

Adding 2 negative numbers ➡➡positive result

$$\begin{array}{r} \phantom{0000}1 \phantom{00}1 \\ -6 \phantom{0000}1010 \\ + -6 \phantom{0000}1010 \\ \hline \phantom{00}4 \phantom{0000}\cancel{1}0100 \end{array}$$

# Handling 2's Complement Overflow

- Two cases (look at two most significant carries):

1. 1 carried in (c3), and 0 carried out (c4)

- Only if  $a3 = 0$  and  $b3 = 0$

2. 0 carried in (c3), and 1 carried out (c4)

- Only if  $a3 = 1$  and  $b3 = 1$

c4	c3	c2	c1	c0
	a3	a2	a1	a0
	b3	b2	b1	b0
	s3	s2	s1	s0

n bit two's comp:  $-2^n$   
 $\text{<--->} 2^n - 1$   
 split into pos and neg  
 ranges and find smallest  
 and largest possible  
 results. show that they're  
 in range for twos comp.


a3	b3	c3	c4	s3	overflow
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

sum of  
two pos  
is pos

sum of  
two negs  
is neg
 
# Overflow Computation in Adder/Subtractor

For 2s complement, overflow if 2 most significant carries differ



*= 0 then no overflow,*

*= 1 then overflow*




# Ripple Carry Adder Circuit Depth

Have to wait for the carry to be computed

$$A_3A_2A_1A_0 + B_3B_2B_1B_0 = S_3S_2S_1S_0$$

 - Depth of a circuit is the longest (most gates to go through) path
- Overflow has depth 8
- $S_3$  has depth 7
- In general,  $S_i$  has depth  $2i+1$  in Ripple-Carry Adder



# Carry Lookahead Adder (CLA)

Goal: produce an adder circuit of shorter depth

Mechanism: rewrite the carry function

$$C_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$C_{i+1} = a_i b_i + c_i (a_i + b_i)$$

$$C_{i+1} = g_i + c_i (p_i)$$

Generates carry out ( $c_{i+1}=1$ )  
if  $a_i = b_i = 1$

carry generate  
 $g_i = a_i b_i$

Propagates carry in ( $c_i = 1$ )  
If either  $a_i = 1$  or  $b_i = 1$

carry propagate  
 $p_i = a_i + b_i$

Now, look at  $g_i$  and  $p_i$

They both use **only**  $a_i$  and  $b_i$ , neither depend on the carry. If we write the carry function in terms of  $g_i$  and  $p_i$  we might avoid waiting for the carry.

# Carry Lookahead Adder (CLA)

Recursively define carries in terms of propagate and generate signals

$$C_1 = g_0 + C_0 p_0$$

$$C_2 = g_1 + C_1 p_1$$

$$= g_1 + (g_0 + C_0 p_0) p_1$$

$$= g_1 + g_0 p_1 + C_0 p_0 p_1$$

$$C_3 = g_2 + C_2 p_2$$

$$= g_2 + (g_1 + g_0 p_1 + C_0 p_0 p_1) p_2$$

$$= g_2 + g_1 p_2 + g_0 p_1 p_2 + C_0 p_0 p_1 p_2$$

**We can compute carries in terms of  $a_i$ 's,  $b_i$ 's and  $c_0$ .**  
This bits are available right away, we don't have to wait for them.

$i^{\text{th}}$  carry has  $i+1$  product terms, the largest of which has  $i+1$  literals

Carry circuit depth is 3 (SoP form)

If gates take 2 inputs, total circuit depth is  $1 + \log_2(k)$  for  $k$ -bit addition

# Carry Lookahead Adder (CLA)

$$C_0 = 0$$

$$C_1 = g_0 + C_0 p_0$$

$$C_2 = g_1 + g_0 p_1 + C_0 p_0 p_1$$

$$C_3 = g_2 + g_1 p_2 + g_0 p_1 p_2 + C_0 p_0 p_1 p_2$$

$$C_4 = g_3 + g_2 p_3 + g_1 p_2 p_3 + g_0 p_1 p_2 p_3 + C_0 p_0 p_1 p_2 p_3$$


$$S_0 = a_0 \oplus b_0 \oplus C_0$$

$$S_1 = a_1 \oplus b_1 \oplus C_1$$

$$S_2 = a_2 \oplus b_2 \oplus C_2$$

$$S_3 = a_3 \oplus b_3 \oplus C_3$$

$$S_4 = a_4 \oplus b_4 \oplus C_4$$

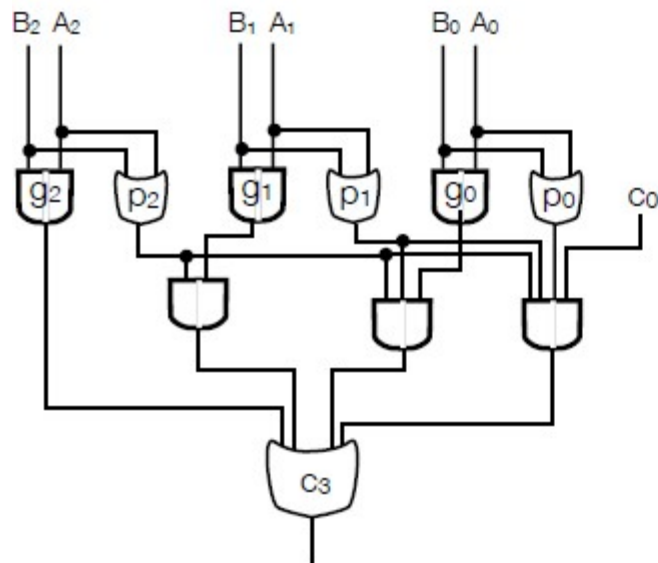

Depth of 3 for all  $c_i$

Depth of 4 for all  $s_i, i > 0$

Note: gates take only 2 inputs: depth increases by a  $\log_2$  factor: still much less than linear of ripple-carry adder

# Sequential circuits

# Now on to Sequential Circuits

We've seen that gates are the building blocks for combinational circuits, now we'll see how latches and flip-flops are the building blocks of sequential circuits.

- Gates: built from transistors
- Latches: built from gates
- Flip-flops: built from latches

Difference between latches and flip-flops:

- Latches do not have clock signals

Latches

- Set/Reset
- D

Flip-flops

- D
- T
- Enabled
- Resettable

Registers


Counters

# How are Sequential Circuits different from Combinational Circuits?

- How to make a circuit out of gates that is not combinational?
  - Feed-back: create loops in the diagram
  - Outputs of sequential logic depend on both current and prior values – **it has memory**
- Definitions:
  - **State**: all the information about a circuit to explain its future behavior
  - **Latches and flip-flops**: state elements that store one bit of state
  - **Synchronous sequential elements**: combinational logic followed by a bank of flip-flops
 
# Bistable Circuits (Static latch)

- Fundamental building blocks of other elements
  - it can remember the state of the circuit indefinitely
- No inputs
- Two outputs ( $Q$  and  $Q'$ )






# Bistable Circuit Analysis


Consider all the cases

- Consider the two possible cases:

 - $Q = 0$ : then  $\bar{Q} = 1$  and  $Q = 0$  (consistent)



 
- $Q = 1$ : then  $\bar{Q} = 0$  and  $Q = 1$  (consistent)



- Bistable circuit stores 1 bit of state ( $Q$ , or  $Q'$ )
- But there are no inputs to control state

# Set/Reset Latch

A latch with NOR gates

 

•  $S = 1, R = 0$


•  $S = 0, R = 1$

•  $S = 0, R = 0$

•  $S = 1, R = 1$

# S/R Latch Analysis


- $S = 1, R = 0$ : then  $Q = 1$

 

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

set



- $S = 0, R = 1$ : then  $Q = 0$

 

reset

# S/R Latch Analysis


- $S = 0, R = 0$ : then  $Q = Q_{prev}$

  

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

memory!

 - $S = 1, R = 1$ : then  $Q = 0$  and  $\overline{Q} = 0$




$Q = \overline{Q}$   
Invalid state

# S/R Latch Symbol


- Set operation
  - makes output 1 ( $S = 1, R = 0, Q = 1$ )
- Reset operation
  - makes output 0 ( $S = 0, R = 1, Q = 0$ )
- What about invalid state? ( $S = 1, R = 1$ )  
makes  $Q = \bar{Q} = 0$

SR Latch  
Symbol

 
 
# S/R Latch with Enable


- The SR latch is sensitive to its inputs all the time. It is sometimes useful to be able to disable the inputs.
- The *SR latch with enable* accomplishes this by adding an enable input,  $C$ , to the original implementation of the latch that allows the latch to be enabled or disabled.




- The SR latch with enable is still sensitive to  $S = R = 1$
 
# D Latch


- Prevents  $S = R = 1$  by adding an inverter
- The D latch has two inputs (C and D)
  - C (control input): controls when the output changes
  - D (data input): controls what the output changes to
- When  $C = 1$ , D passes through to Q (transparent latch)
- When  $C = 0$ , Q holds previous value (opaque latch)



D Latch  
Symbol

 

# D Latch Internal Circuit

 

C	D	$\overline{D}$	S	R	Q	$\overline{Q}$	
0	X	X	0	0	Prev	Prev	No change
1	0	1	0	1	0	1	Reset
1	1	0	1	0	1	0	Set

Copyright © 2007 Elsevier

- Level-sensitive: output follows the input as long as it is enabled ( $C=1$ )
- If D changes while  $C=1$  the output will reflect D (transparent)




# How to Coordinate Multiple Components of a Circuit?

- To do computations, we need more than just combinational circuits We need to use past circuit state to influence future output (latches)
- But how do we coordinate computations and the changing of state values across lots of different parts of a circuit?
  - How to synchronize latches to change values at the same time?
- We use CLOCKING (eg. 1 GHz clock on Intel processors)
- **On each clock pulse, combinational computations are performed, and results stored in latches**
- How to introduce clocks into latches?
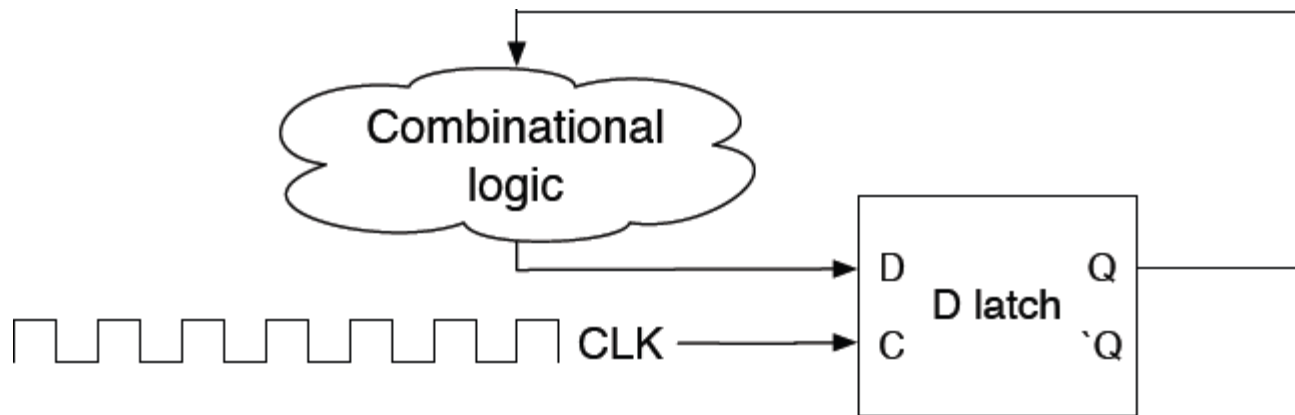
# Flip-flops: Latches on a Clock


- A straightforward latch is not safely synchronous (or predictably synchronous)
  - Flip-flops can have its state changed only at a single, known instant of time.



- Flip-flops designed so that outputs will NOT change within a single clock pulse
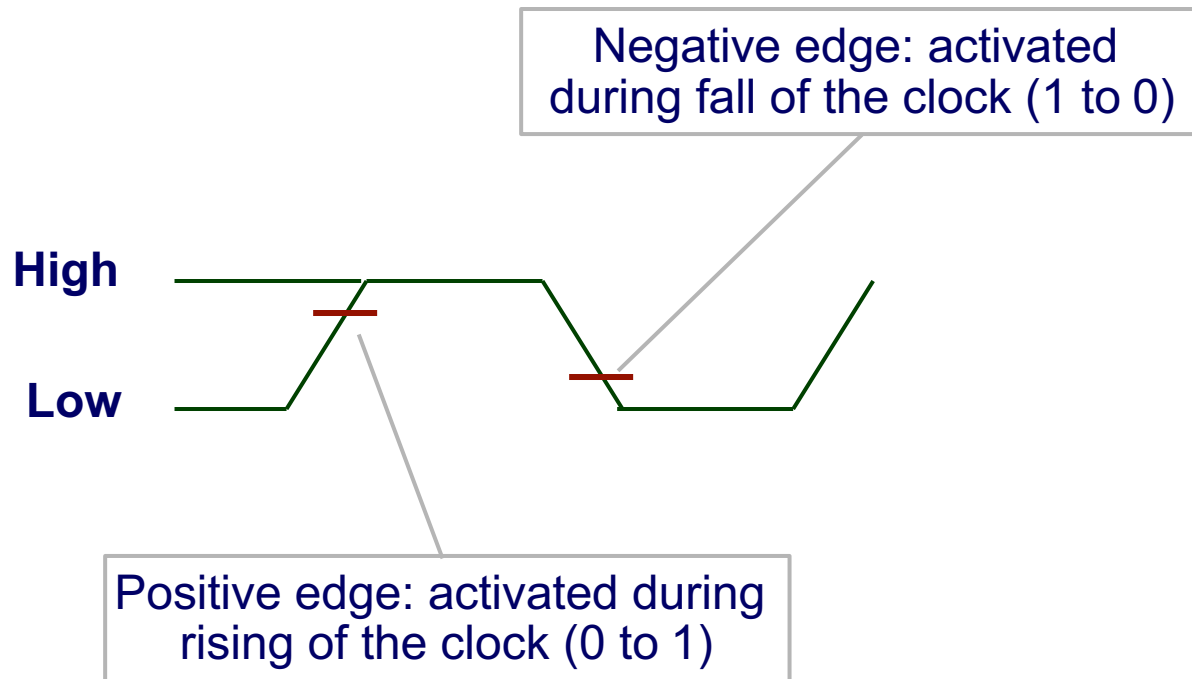
# Flip-Flop


- Sensitive to the edge (transition) of the clock
  - rising or falling of the clock



# Positive Edge-Triggered D Flip-Flop

- Two inputs:
  - Clk, D
- Function
  - The flip-flop samples D on rising edge of the Clk
    - When Clk goes from 0 to 1, D passes through Q
  - Otherwise, Q holds its value
  - Q only changes on rising edge of the Clk
- A flip-flop is called “edge-triggered” because it is activated only on the clock edge


D Flip-Flop  
Symbols

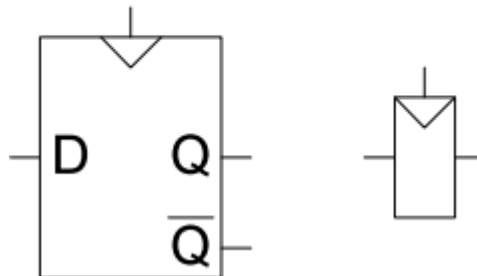




# Negative Edge-Triggered D Flip-Flop

- Two inputs:
  - Clk, D
- Function
  - The flip-flop samples D on the falling edge of Clk
    - When Clk falls from 1 to 0, D passes through to Q
  - Otherwise, Q holds its previous values
  - Q changes only on the falling edge of Clk
- A flip-flop is called an edge-triggered device because it is activated on a clock cycle

D Flip-Flop  
Symbols

 


# Flip-Flop versus Latch

 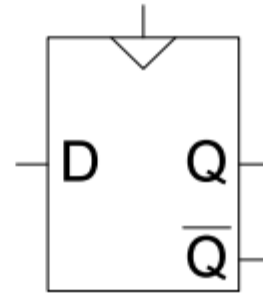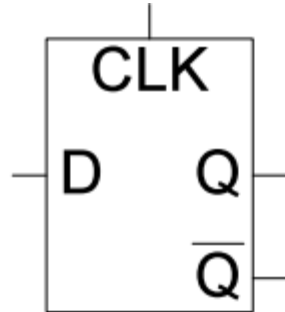



Latch outputs change at any time, flip-flops only during clock transitions

# Master Slave D Flip-Flop

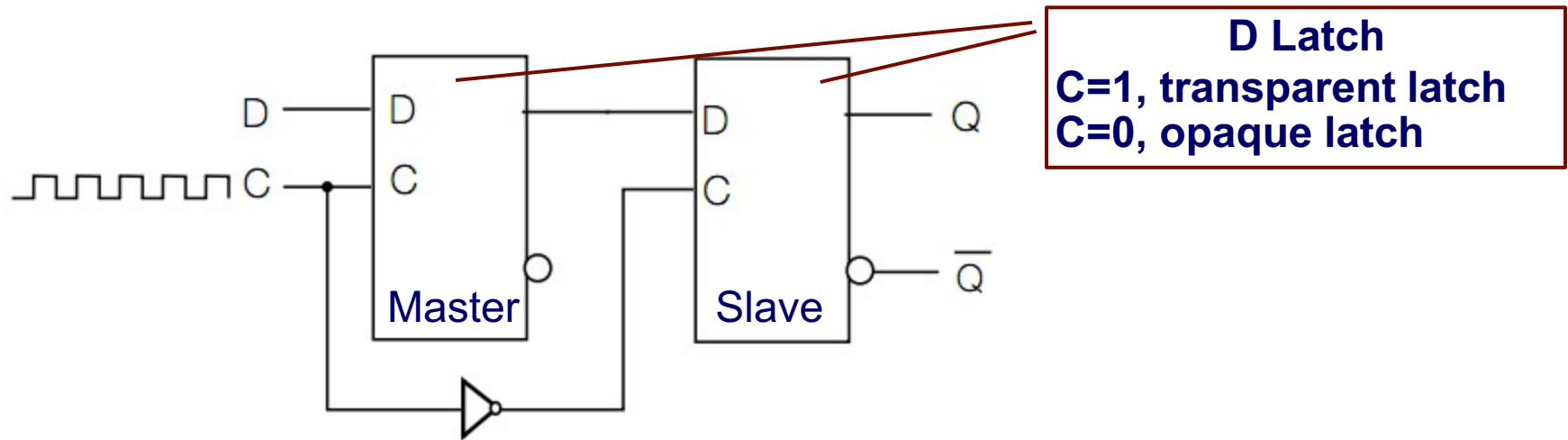

- C (Control) is fed a clock pulse (alternates between 0 and 1 with fixed period)
  - C=1: Master latch “on”, Slave latch “off”
    - New D input read into master
    - Previous Q values still emitted (not affected by new D inputs)
  - C=0: Master latch “off”, Slave latch “on”
    - Changing D inputs has no effect on Master (or Slave) latch
    - D inputs from last time C=1 stored safely in Master and transferred into Slave and reflected on output Q

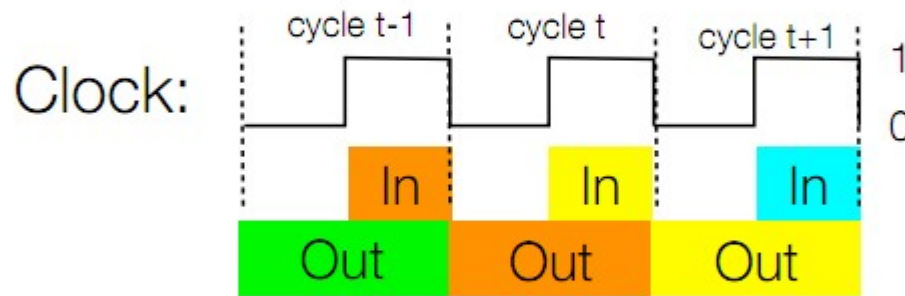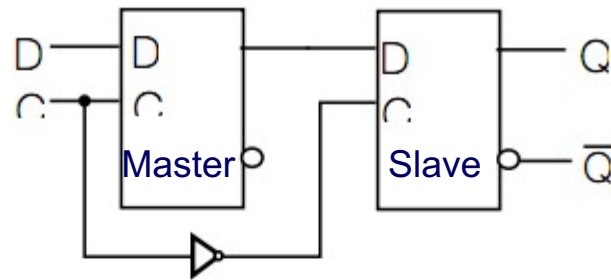
# Master Slave D Flip-Flop Activation Time



- $Q(t)$ : value output by Flip-Flop during the  $t^{\text{th}}$  clock cycle (clock =0, then 1 during a full cycle)
- Depends on input during end of  $t-1^{\text{st}}$  cycle




# Bit Storage Summary

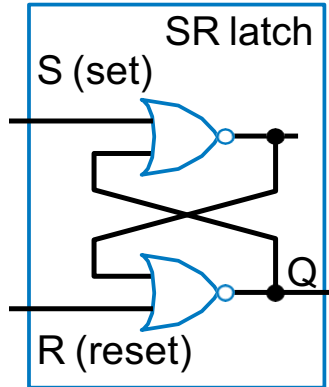


**Feature:**  $S=1$  sets  $Q$  to 1,  $R=1$  resets  $Q$  to 0.

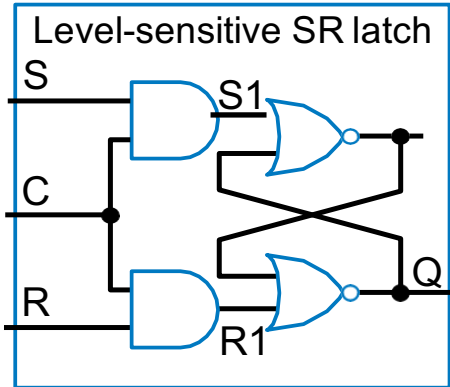**Problem:**  $SR=11$  yields undefined  $Q$ , other glitches may set/reset inadvertently.




**Feature:**  $S$  and  $R$  only have effect when  $C=1$ . An external circuit can prevent  $SR=11$  when  $C=1$ .

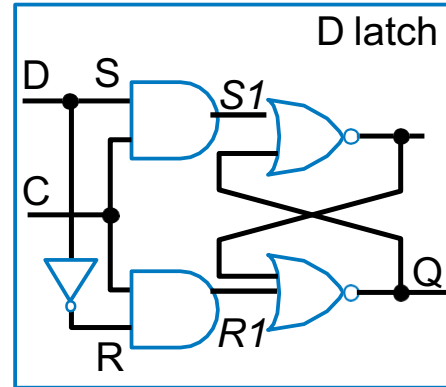**Problem:** avoiding  $SR=11$  can be a burden.



**Feature:**  $SR$  can't be 11.

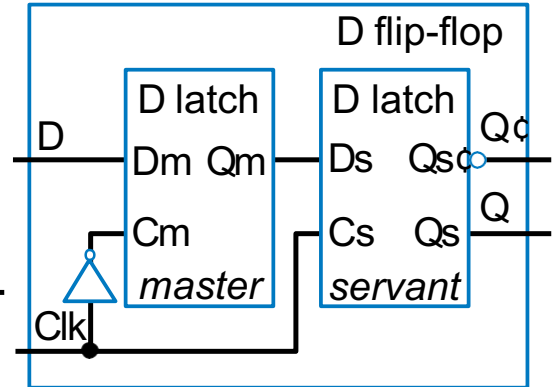**Problem:**  $C=1$  for too long will propagate new values through too many latches; for too short may not result in the bit being stored.





**Feature:** Only loads  $D$  value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle.

**Tradeoff:** uses more gates internally, and requires more external gates than  $SR$ — but transistors today are more plentiful and cheaper.

We considered increasingly better bit storage until we arrived at the robust D flip-flop bit storage

# Registers

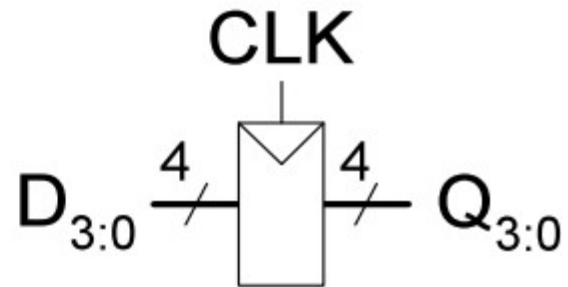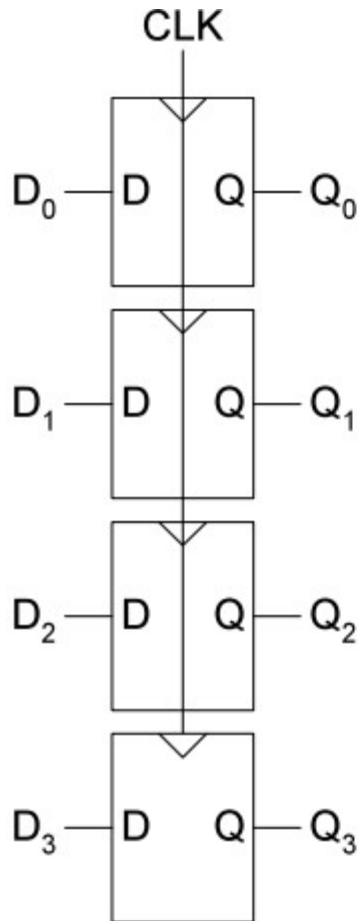


# Synchronous Sequential Logic Design

- Structures that can process and store information
  - Registers contain the state of the system
  - Combinational circuits process information
- State changes at the clock edge, so the system is synchronized to the clock
- Rules of synchronous sequential circuit composition:
  - Every circuit is either a register or a combinational circuit
  - At least one circuit element is a register
  - All registers receive the same clock signal
  - Every cyclic path contains one register
- Two common synchronous sequential circuits
  - Finite state machines (FSMs)
  - Pipelines


# Finite State Machines

- A mathematical model of computation used to design:
  - Computer programs
  - Sequential logic circuits
- FSM = State register + combinational logic

 **Stores the next state and loads the next state at clock edge**




 **Computes the next state and computes the outputs**




 
# Finite State Machines

- Can be represented using a state diagram
  - Finite number of states
  - Transitions



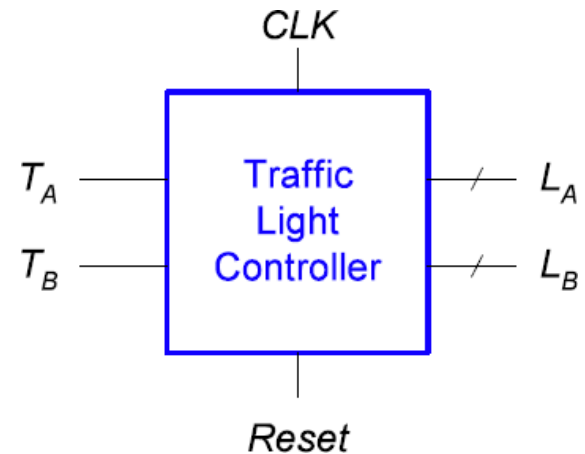 
# FSM: Traffic Light Controller Example

- Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there is traffic)
- Lights:  $L_A$ ,  $L_B$



# FSM State Transition Diagram


- States: Circles
- Transitions: Arcs

 
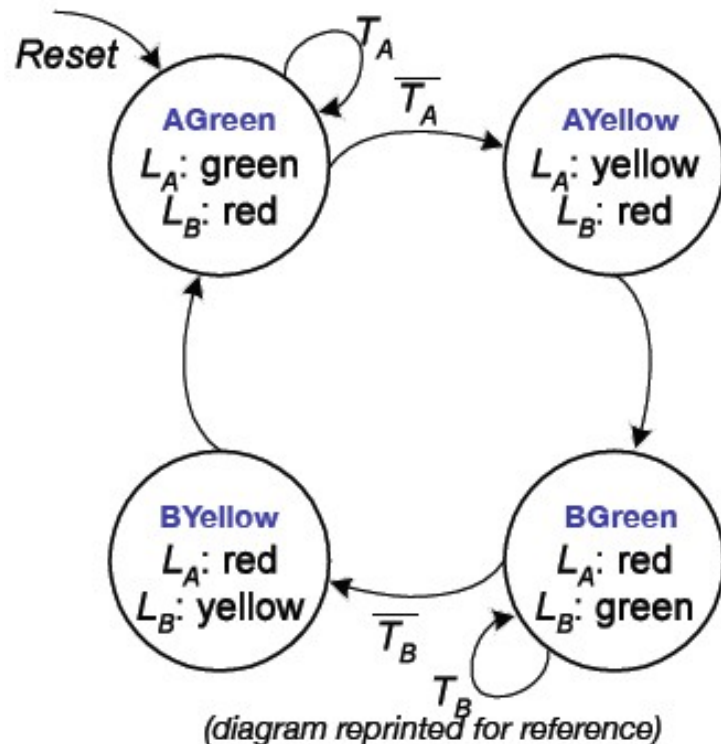
# FSM State Transition Table

- State transitions from diagram can be rewritten in a state transition table

( $S$  = current state,  $S'$  = next state)



Current State	Inputs		Next State
S	TA	TB	S'
AGreen	0	X	AYellow
AGreen	1	X	AGreen
AYellow	X	X	BGreen
BGreen	X	0	BYellow
BGreen	X	1	BGreen
BYellow	X	X	AGreen



# Encoded State Transition Table

- After selecting a state encoding, the symbolic states in the transition table can be realized with current state/next state bits

State	Encoding	
	S1	S0
AGreen	0	0
AYellow	0	1
BGreen	1	0
BYellow	1	1

Current State	Encoded Current State		Inputs		Next State	Encoded Next State	
S	S1	S0	TA	TB	S'	S1'	S0'
AGreen	0	0	0	X	AYellow	0	1
AGreen	0	0	1	X	AGreen	0	0
AYellow	0	1	X	X	BGreen	1	0
BGreen	1	0	X	0	BYellow	1	1
BGreen	1	0	X	1	BGreen	1	0
BYellow	1	1	X	X	AGreen	0	0

# Computing Next State Logic

Current State	Encoded Current State		Inputs		Next State	Encoded Next State	
S	S1	S0	TA	TB	S'	S1'	S0'
AGreen	0	0	0	X	AYellow	0	1
AGreen	0	0	1	X	AGreen	0	0
AYellow	0	1	X	X	BGreen	1	0
BGreen	1	0	X	0	BYellow	1	1
BGreen	1	0	X	1	BGreen	1	0
BYellow	1	1	X	X	AGreen	0	0

- From K-maps, figure out expressions for the next state:
  - $S1(t+1) = S1(t) \text{ xor } S0(t)$
  - $S0(t+1) = \overline{S1(t)} \overline{S0(t)} \overline{TA} + S1(t) \overline{S0(t)} \overline{TB}$
- Another way of writing the same thing (just a change of notation):
  - $S1' = S1 \text{ XOR } S0$
  - $S0' = S1 \wedge S0 \wedge TA \wedge + S1 S0 \wedge TB \wedge$

# FSM Output Table

- FSM output logic is computed in similar manner as next state logic
- In this system, output is a function of current state (Moore machine)
- Alternative – Mealy machine (output function of both current state and inputs, though we won't cover this in class)

*output encoding*

Output	Encoding	
Green	0	0
Yellow	0	1
Red	1	0

*output truth table*

State	State		LA		LB	
	S1	S0	LA1	LA0	LB1	LB0
AGreen	0	0	0	0	1	0
AYellow	0	1	0	1	1	0
BGreen	1	0	1	0	0	0
BYellow	1	1	1	0	0	1


- Compute output bits as function of state bits

$$LA1 = S1; LA0 = S1'S0$$

$$LB1 = 'S1; LB0 = S1S0$$


*red light*

# State Register: Assume D Flip-Flop

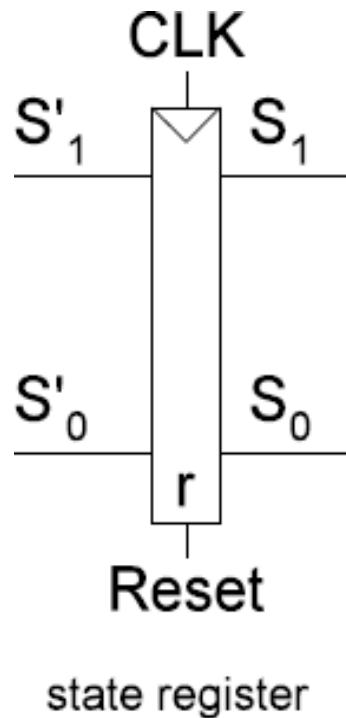
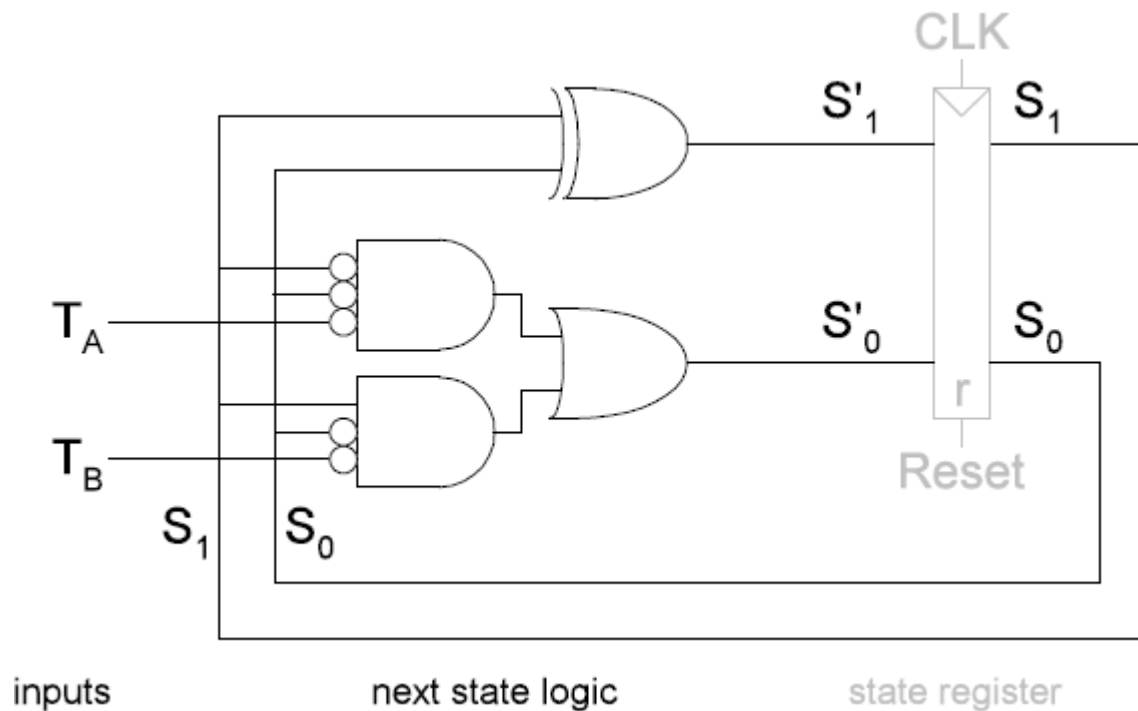
# FSM: Figure out Next State Logic


- $S_1' = S_1 \text{ XOR } S_0$
- $S_0' = S_1 \wedge S_0 \wedge T_A \vee S_1 S_0 \wedge T_B$



# FSM: Figure out Output Logic

$$LA1 = S1; LA0 = S1'S0$$

$$LB1 = \neg S1; LB0 = S1S0$$

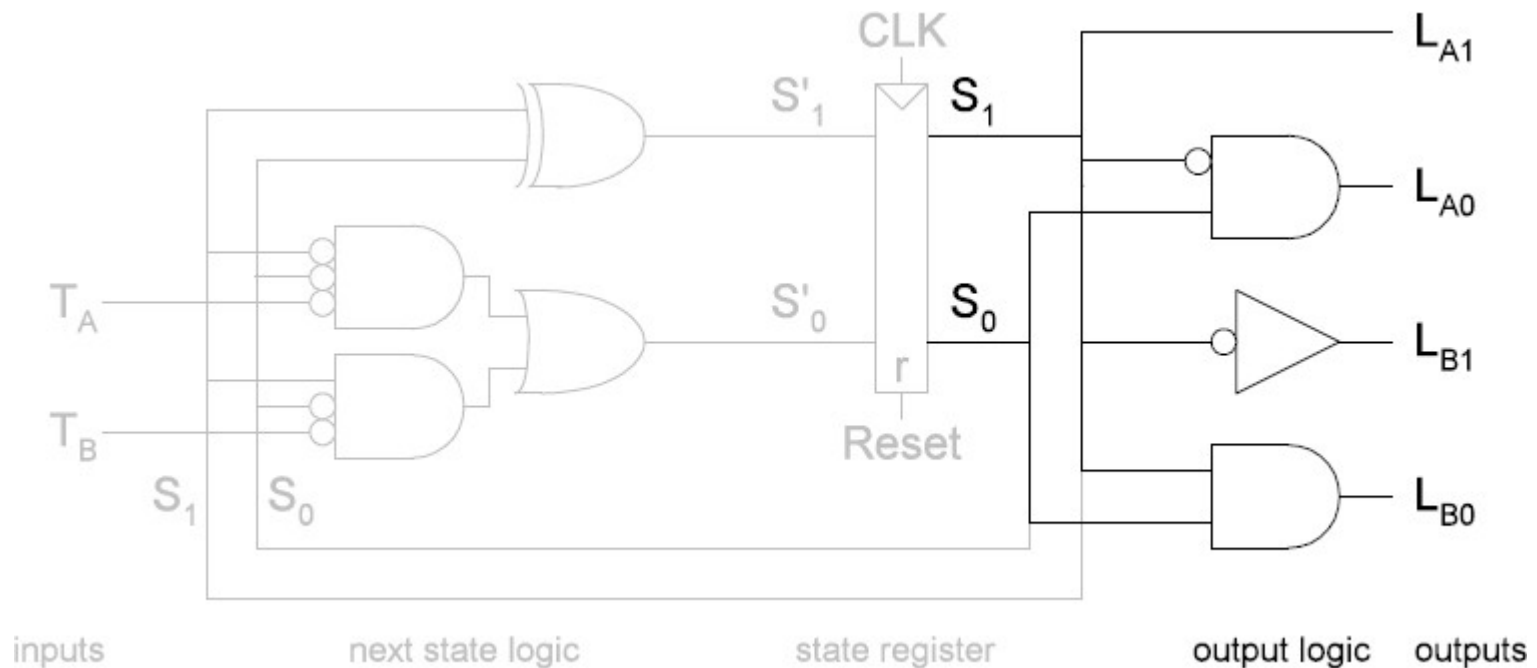

# FSM: divisible by 3

- Construct a "divisible by 3" FSM that accepts a binary number entered 1 bit at a time, MSB first, and indicate with a light if the number entered so far is divisible by 3.

1)  $N \bmod 3$

$$0 \rightarrow N = 3p + 0$$

$$1 \rightarrow N = 3p + 1$$

$$2 \rightarrow N = 3p + 2$$

2) If the number so far is  $N$ , after a digit  $b$  is entered, the new number is  $N' = 2N + b$

$N \bmod 3$

$$1 \rightarrow N = 3p + 0, \text{ after digit } b \text{ is entered, } N' = 6p + b.$$

$$N' = b \bmod 3$$

$$2 \rightarrow N = 3p + 1, \text{ after digit } b \text{ is entered, } N' = 6p + 2 + b.$$


$$N' = b + 2 \bmod 3$$

$$2 \rightarrow N = 3p + 2, \text{ after digit } b \text{ is entered, } N' = 6p + 4 + b.$$

$$N' = b + 1 \bmod 3$$

# FSM: divisible by 3

## 1. State Transition Diagram

 

## 2. State Transition Table

S1	S0	b	S1'	S0'	light
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	0	0

## 2. State Encoding

State	S1	S0
0	0	0
1	0	1
2	1	0

## 3. Next State Logic

$$S1' = \overline{S1} \overline{S0} \overline{b} + S1 \overline{S0} b$$

$$S0' = \overline{S1} \overline{S0} b + S1 \overline{S0} \overline{b}$$

## 4. Output Logic

$$\text{light} = \overline{S1} \overline{S0}$$