

# Lecture 14:

## Final Lecture

# Announcements


- Project 3 due tomorrow
  - Due August 11<sup>th</sup> 11:55pm
  - Due day before Final, so plan accordingly
  - No Extension
  - Max point: 120, not 130
- Final is on Wednesday
  - 3-hour timed exam
  - Open for 24-hours
  - Few Sample Questions just released
- Remember to take the instructional survey
  - Currently ~70% of the class has taken it.
  - If at least 95% of the class takes it, one point will be added after final grade calculations
  - ~22 more students need to take it.
- Lecture today:
  - Finishing up FSM and Sequential Circuits
- Rest of Lecture/Recitation
  - Questions on any of the material from the whole course, questions on PA3

# How are Sequential Circuits different from Combinational Circuits?

- How to make a circuit out of gates that is not combinational?
  - Feed-back: create loops in the diagram
  - Outputs of sequential logic depend on both current and prior values – **it has memory**
- Definitions:
  - **State**: all the information about a circuit to explain its future behavior
  - **Latches and flip-flops**: state elements that store one bit of state
  - **Synchronous sequential elements**: combinational logic followed by a bank of flip-flops

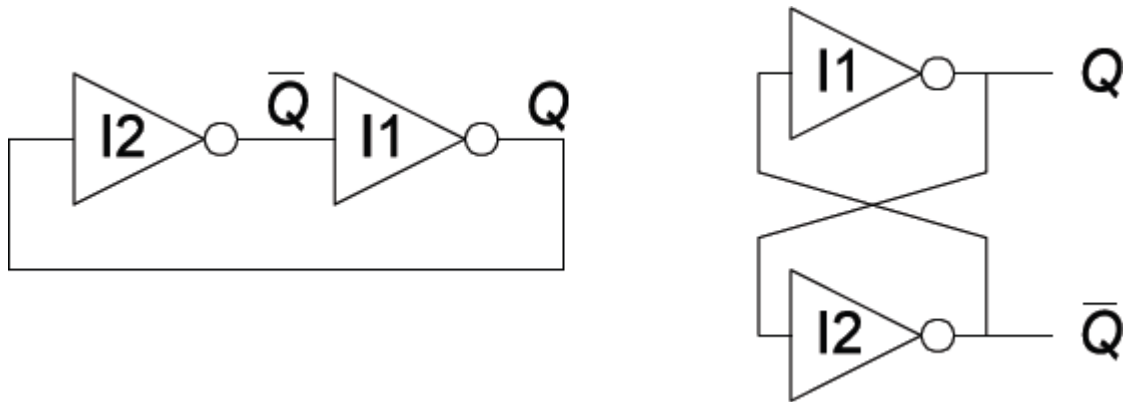
# Bistable Circuits (Static latch)

- Fundamental building blocks of other elements
  - it can remember the state of the circuit indefinitely
- No inputs
- Two outputs ( $Q$  and  $Q'$ )



# Set/Reset Latch

A latch with NOR gates

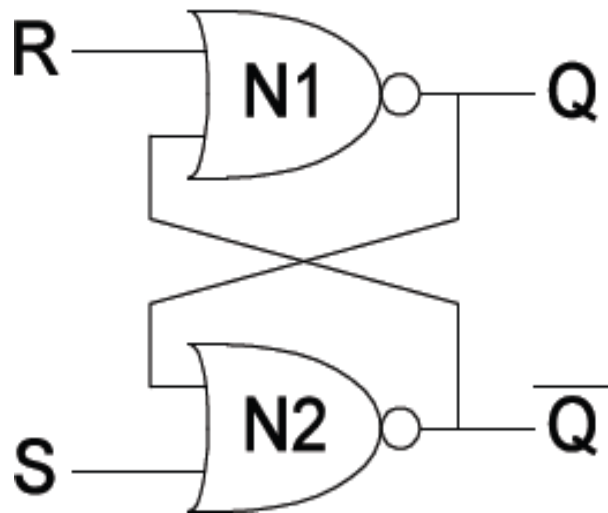

•  $S = 1, R = 0$

•  $S = 0, R = 1$


•  $S = 0, R = 0$

•  $S = 1, R = 1$

# S/R Latch Symbol


- Set operation
  - makes output 1 ( $S = 1, R = 0, Q = 1$ )
- Reset operation
  - makes output 0 ( $S = 0, R = 1, Q = 0$ )
- What about invalid state? ( $S = 1, R = 1$ )  
makes  $Q = \bar{Q} = 0$

SR Latch  
Symbol

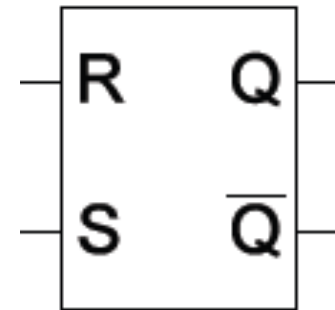
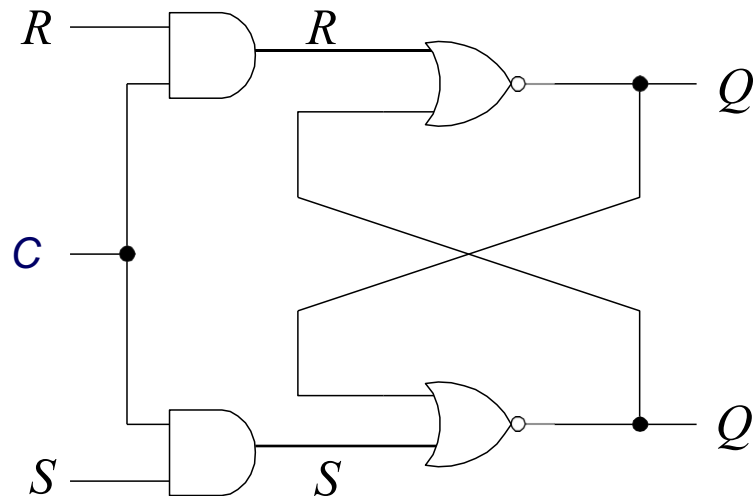
# S/R Latch with Enable


- The SR latch is sensitive to its inputs all the time. It is sometimes useful to be able to disable the inputs.
- The *SR latch with enable* accomplishes this by adding an enable input,  $C$ , to the original implementation of the latch that allows the latch to be enabled or disabled.




- The SR latch with enable is still sensitive to  $S = R = 1$
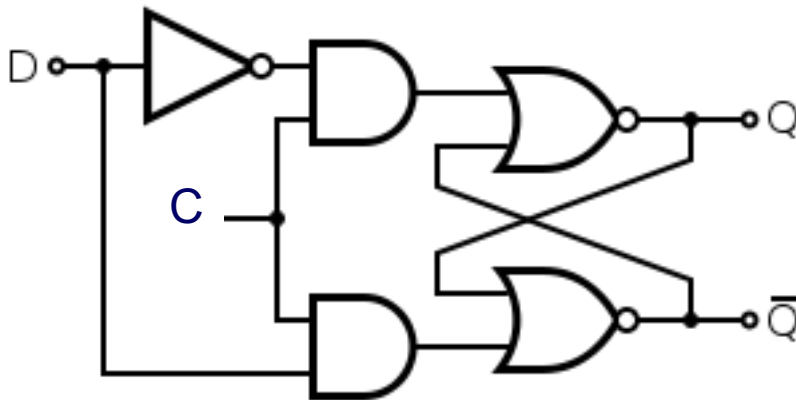
# D Latch

- Prevents  $S = R = 1$  by adding an inverter
- The D latch has two inputs (C and D)
  - C (control input): controls when the output changes
  - D (data input): controls what the output changes to
- When  $C = 1$ , D passes through to Q (transparent latch)
- When  $C = 0$ , Q holds previous value (opaque latch)



D Latch  
Symbol

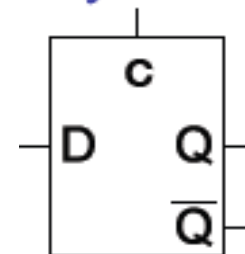




# How to Coordinate Multiple Components of a Circuit?

- To do computations, we need more than just combinational circuits We need to use past circuit state to influence future output (latches)
- But how do we coordinate computations and the changing of state values across lots of different parts of a circuit?
  - How to synchronize latches to change values at the same time?
- We use CLOCKING (eg. 1 GHz clock on Intel processors)
- **On each clock pulse, combinational computations are performed, and results stored in latches**
- How to introduce clocks into latches?
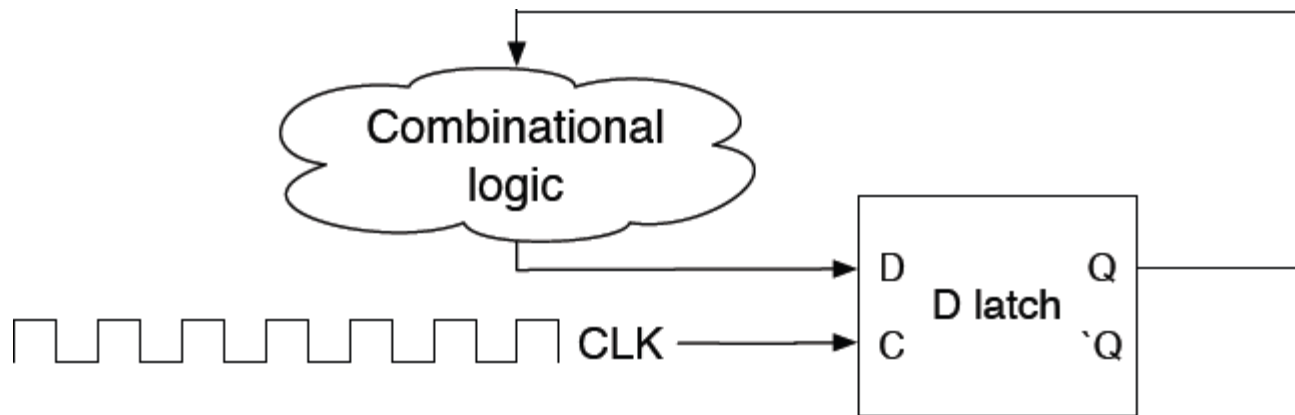
# Flip-flops: Latches on a Clock


- A straightforward latch is not safely synchronous (or predictably synchronous)
  - Flip-flops can have its state changed only at a single, known instant of time.



- Flip-flops designed so that outputs will NOT change within a single clock pulse
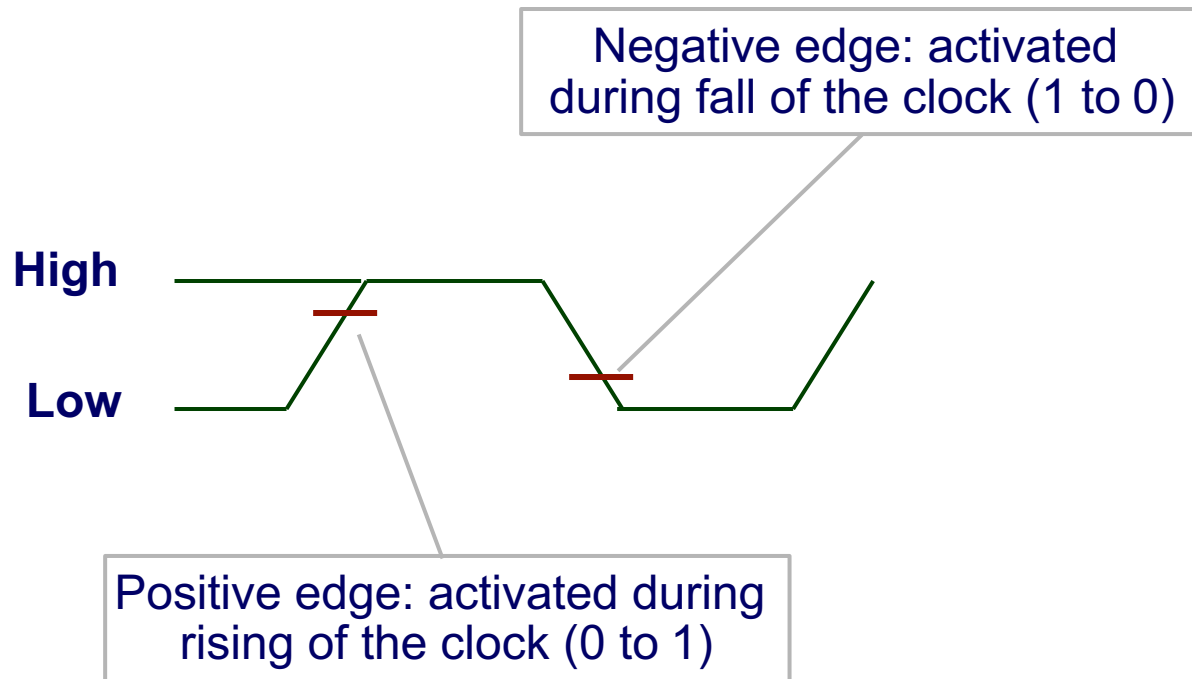
# Flip-Flop


- Sensitive to the edge (transition) of the clock
  - rising or falling of the clock



# Positive Edge-Triggered D Flip-Flop

- Two inputs:
  - Clk, D
- Function
  - The flip-flop samples D on rising edge of the Clk
    - When Clk goes from 0 to 1, D passes through Q
  - Otherwise, Q holds its value
  - Q only changes on rising edge of the Clk
- A flip-flop is called “edge-triggered” because it is activated only on the clock edge


D Flip-Flop  
Symbols

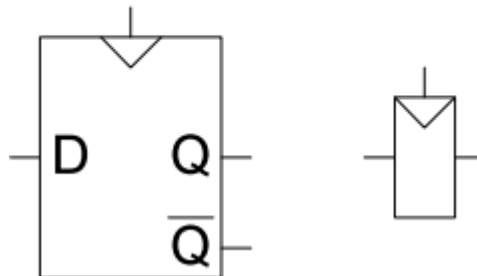




# Negative Edge-Triggered D Flip-Flop

- Two inputs:
  - Clk, D
- Function
  - The flip-flop samples D on the falling edge of Clk
    - When Clk falls from 1 to 0, D passes through to Q
  - Otherwise, Q holds its previous values
  - Q changes only on the falling edge of Clk
- A flip-flop is called an edge-triggered device because it is activated on a clock cycle

D Flip-Flop  
Symbols

 


# Flip-Flop versus Latch

 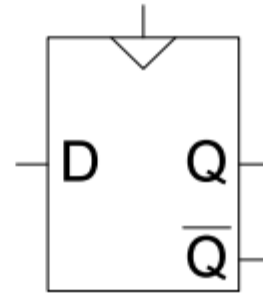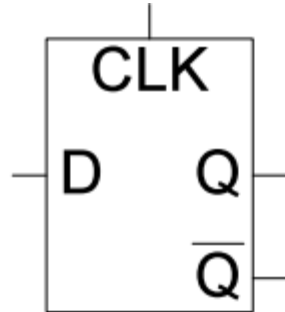



Latch outputs change at any time, flip-flops only during clock transitions

# Master Slave D Flip-Flop

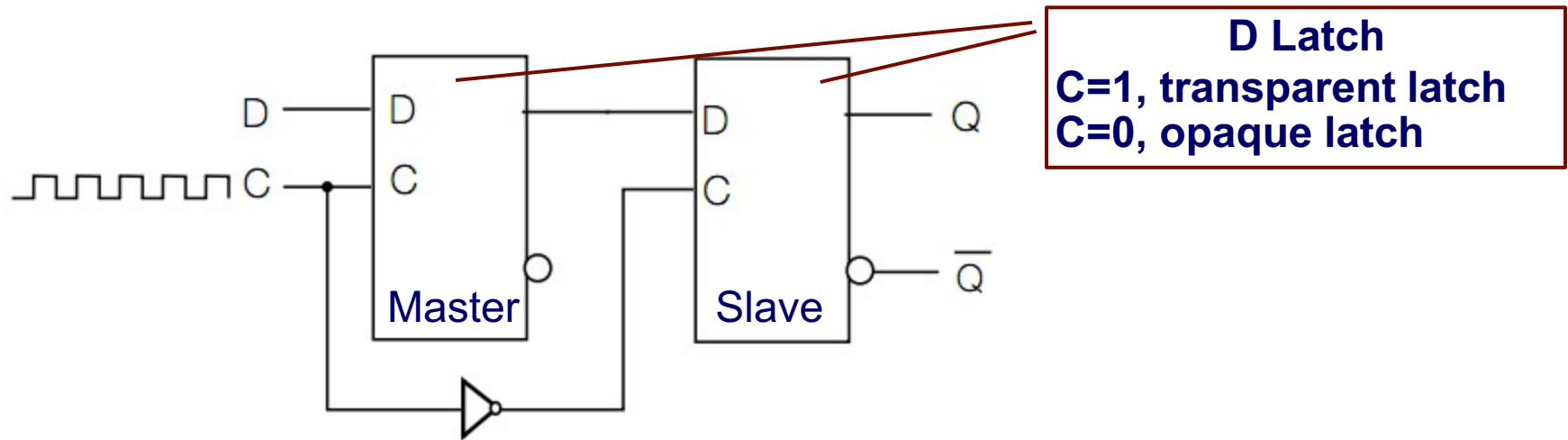

- C (Control) is fed a clock pulse (alternates between 0 and 1 with fixed period)
  - C=1: Master latch “on”, Slave latch “off”
    - New D input read into master
    - Previous Q values still emitted (not affected by new D inputs)
  - C=0: Master latch “off”, Slave latch “on”
    - Changing D inputs has no effect on Master (or Slave) latch
    - D inputs from last time C=1 stored safely in Master and transferred into Slave and reflected on output Q

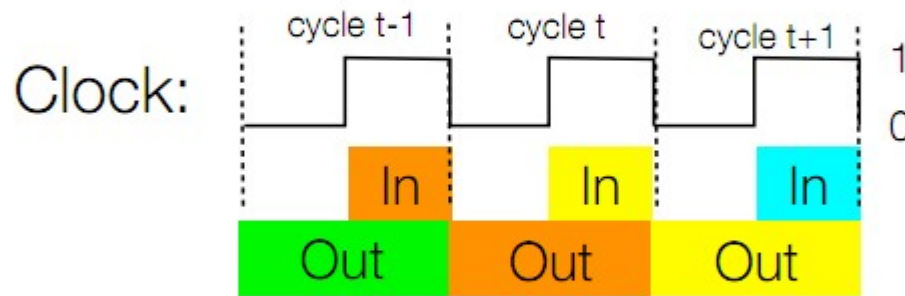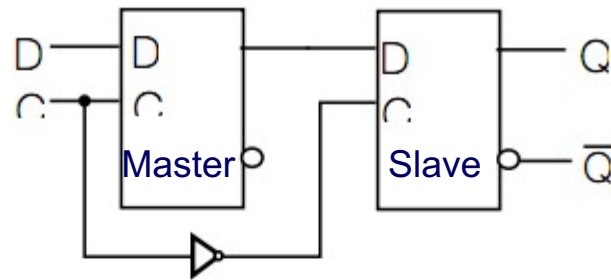
# Master Slave D Flip-Flop Activation Time



- $Q(t)$ : value output by Flip-Flop during the  $t^{\text{th}}$  clock cycle (clock =0, then 1 during a full cycle)
- Depends on input during end of  $t-1^{\text{st}}$  cycle




# Bit Storage Summary

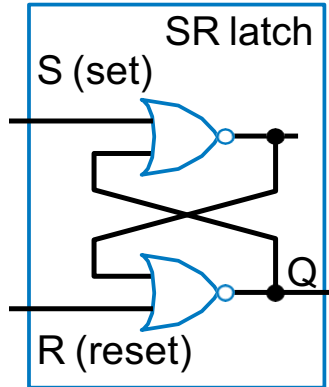


**Feature:**  $S=1$  sets  $Q$  to 1,  $R=1$  resets  $Q$  to 0.

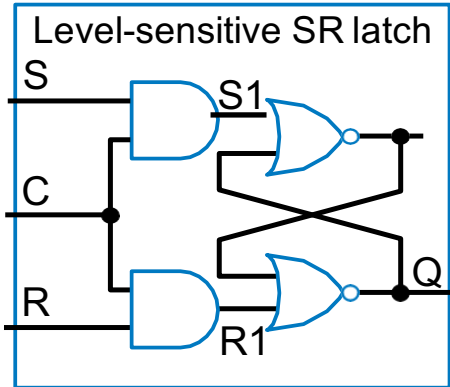**Problem:**  $SR=11$  yields undefined  $Q$ , other glitches may set/reset inadvertently.




**Feature:**  $S$  and  $R$  only have effect when  $C=1$ . An external circuit can prevent  $SR=11$  when  $C=1$ .

 **Problem:** avoiding  $SR=11$  can be a burden.



**Feature:**  $SR$  can't be 11.

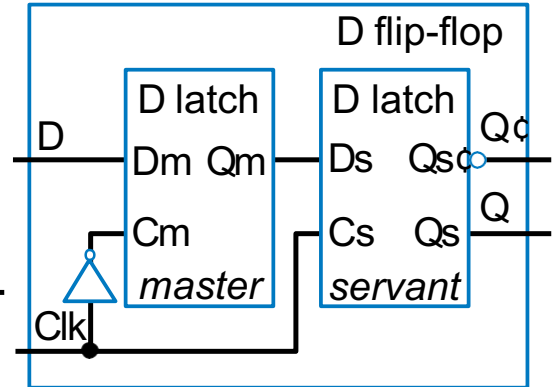**Problem:**  $C=1$  for too long will propagate new values through too many latches; for too short may not result in the bit being stored.





**Feature:** Only loads  $D$  value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle.

**Tradeoff:** uses more gates internally, and requires more external gates than  $SR$ — but transistors today are more plentiful and cheaper.

We considered increasingly better bit storage until we arrived at the robust D flip-flop bit storage

# Registers

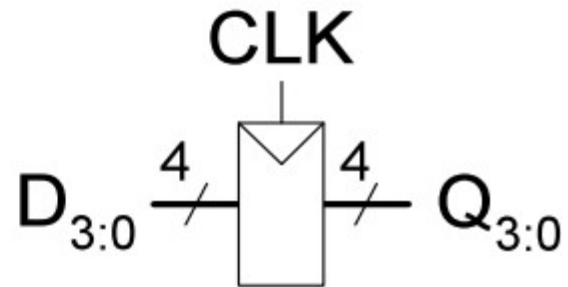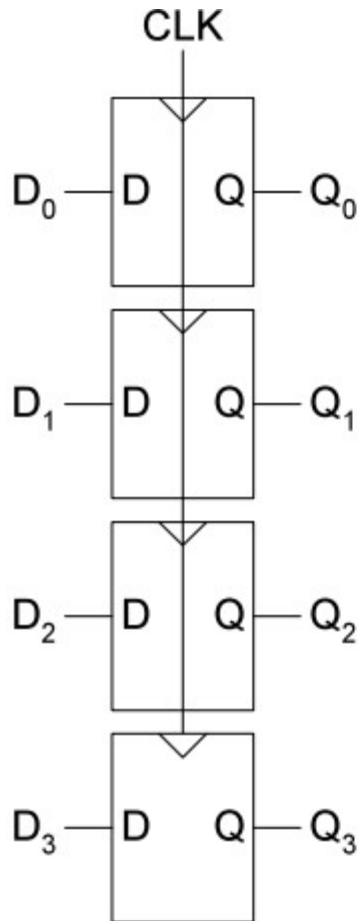


# Synchronous Sequential Logic Design

- Structures that can process and store information
  - Registers contain the state of the system
  - Combinational circuits process information
- State changes at the clock edge, so the system is synchronized to the clock
- Rules of synchronous sequential circuit composition:
  - Every circuit is either a register or a combinational circuit
  - At least one circuit element is a register
  - All registers receive the same clock signal
  - Every cyclic path contains one register
- Two common synchronous sequential circuits
  - Finite state machines (FSMs)
  - Pipelines


# Finite State Machines

- A mathematical model of computation used to design:
  - Computer programs
  - Sequential logic circuits
- FSM = State register + combinational logic

 **Stores the next state and loads the next state at clock edge**




 **Computes the next state and computes the outputs**




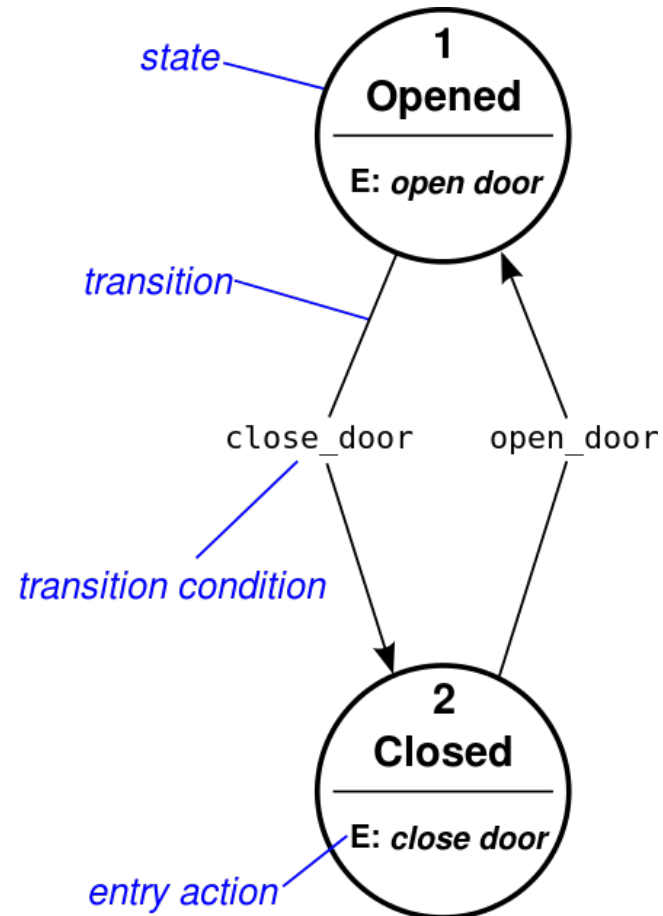
# Finite State Machines

- Can be represented using a state diagram
  - Finite number of states
  - Transitions



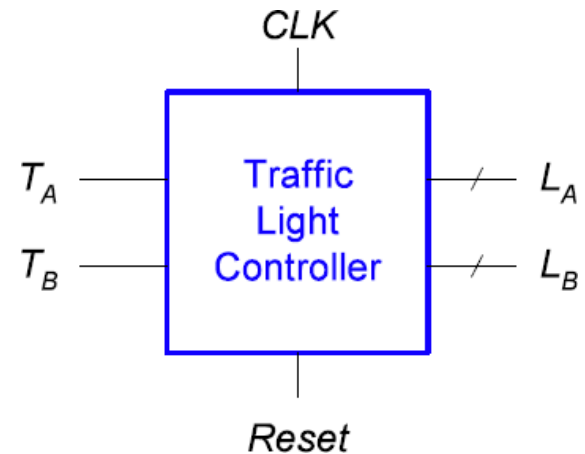 
# FSM: Traffic Light Controller Example

- Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there is traffic)
- Lights:  $L_A$ ,  $L_B$



# FSM State Transition Diagram


- States: Circles
- Transitions: Arcs

 
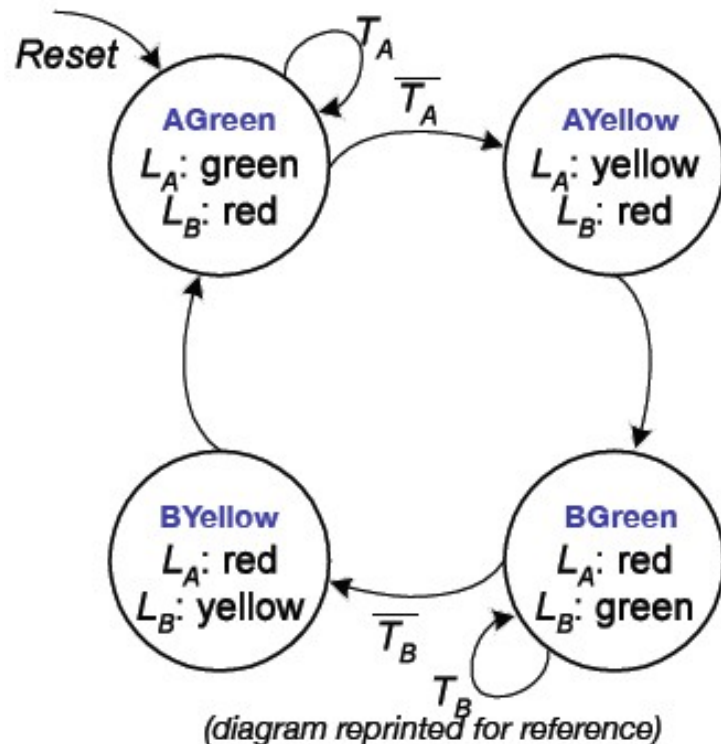
# FSM State Transition Table

- State transitions from diagram can be rewritten in a state transition table

( $S$  = current state,  $S'$  = next state)



Current State	Inputs		Next State
S	TA	TB	S'
AGreen	0	X	AYellow
AGreen	1	X	AGreen
AYellow	X	X	BGreen
BGreen	X	0	BYellow
BGreen	X	1	BGreen
BYellow	X	X	AGreen



# Encoded State Transition Table

- After selecting a state encoding, the symbolic states in the transition table can be realized with current state/next state bits

State	Encoding	
	S1	S0
AGreen	0	0
AYellow	0	1
BGreen	1	0
BYellow	1	1

Current State	Encoded Current State		Inputs		Next State	Encoded Next State	
S	S1	S0	TA	TB	S'	S1'	S0'
AGreen	0	0	0	X	AYellow	0	1
AGreen	0	0	1	X	AGreen	0	0
AYellow	0	1	X	X	BGreen	1	0
BGreen	1	0	X	0	BYellow	1	1
BGreen	1	0	X	1	BGreen	1	0
BYellow	1	1	X	X	AGreen	0	0

# Computing Next State Logic

Current State	Encoded Current State		Inputs		Next State	Encoded Next State	
S	S1	S0	TA	TB	S'	S1'	S0'
AGreen	0	0	0	X	AYellow	0	1
AGreen	0	0	1	X	AGreen	0	0
AYellow	0	1	X	X	BGreen	1	0
BGreen	1	0	X	0	BYellow	1	1
BGreen	1	0	X	1	BGreen	1	0
BYellow	1	1	X	X	AGreen	0	0

- From K-maps, figure out expressions for the next state:
  - $S1(t+1) = S1(t) \text{ xor } S0(t)$
  - $S0(t+1) = \overline{S1(t)} \overline{S0(t)} \overline{TA} + S1(t) \overline{S0(t)} \overline{TB}$
- Another way of writing the same thing (just a change of notation):
  - $S1' = S1 \text{ XOR } S0$
  - $S0' = S1 \wedge S0 \wedge TA \wedge + S1 S0 \wedge TB \wedge$

# FSM Output Table

- FSM output logic is computed in similar manner as next state logic
- In this system, output is a function of current state (Moore machine)
- Alternative – Mealy machine (output function of both current state and inputs, though we won't cover this in class)

*output encoding*

Output	Encoding	
Green	0	0
Yellow	0	1
Red	1	0

*output truth table*

State	State		LA		LB	
	S1	S0	LA1	LA0	LB1	LB0
AGreen	0	0	0	0	1	0
AYellow	0	1	0	1	1	0
BGreen	1	0	1	0	0	0
BYellow	1	1	1	0	0	1


- Compute output bits as function of state bits

$$LA1 = S1; LA0 = S1'S0$$

$$LB1 = 'S1; LB0 = S1S0$$


*red light*

# State Register: Assume D Flip-Flop

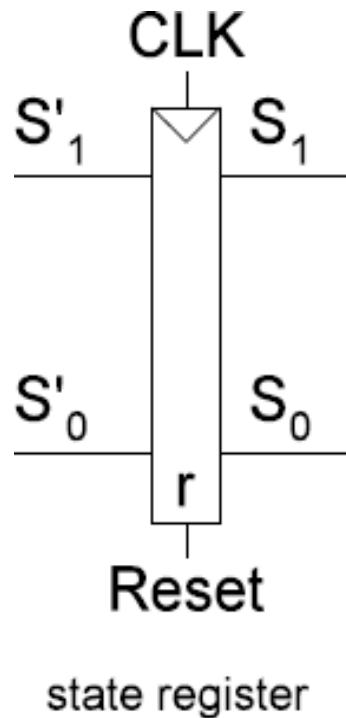
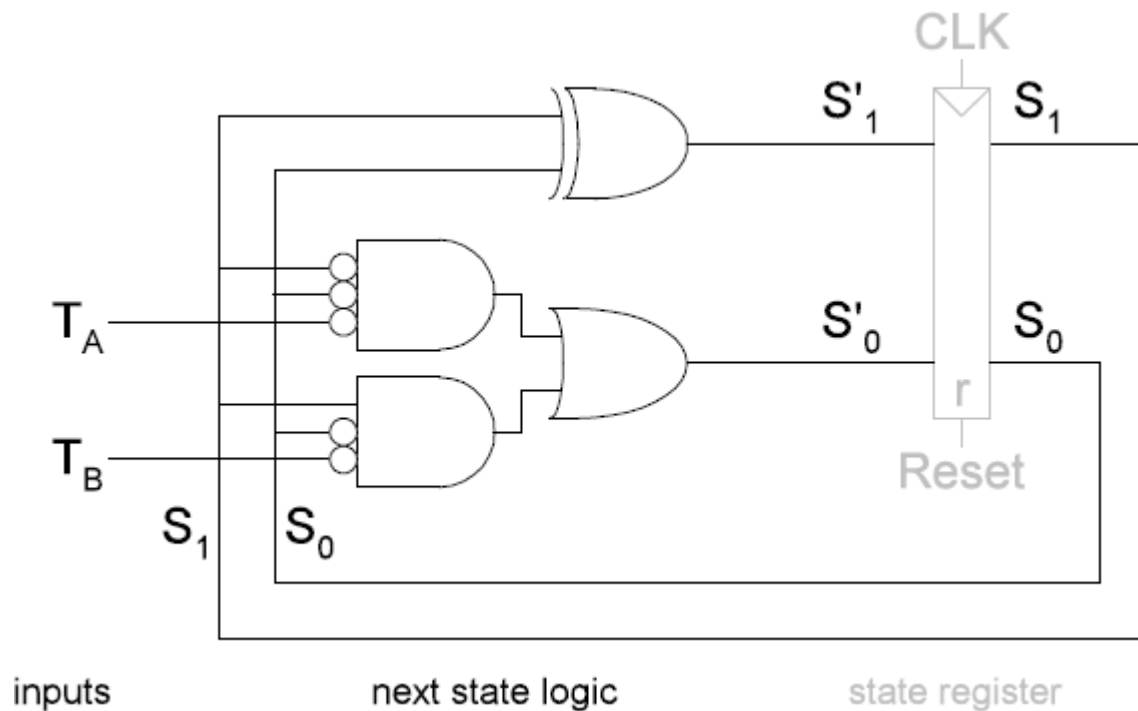
# FSM: Figure out Next State Logic


- $S_1' = S_1 \text{ XOR } S_0$
- $S_0' = S_1 \wedge S_0 \wedge T_A \vee S_1 S_0 \wedge T_B$



# FSM: Figure out Output Logic

$$LA1 = S1; LA0 = S1'S0$$

$$LB1 = \neg S1; LB0 = S1S0$$

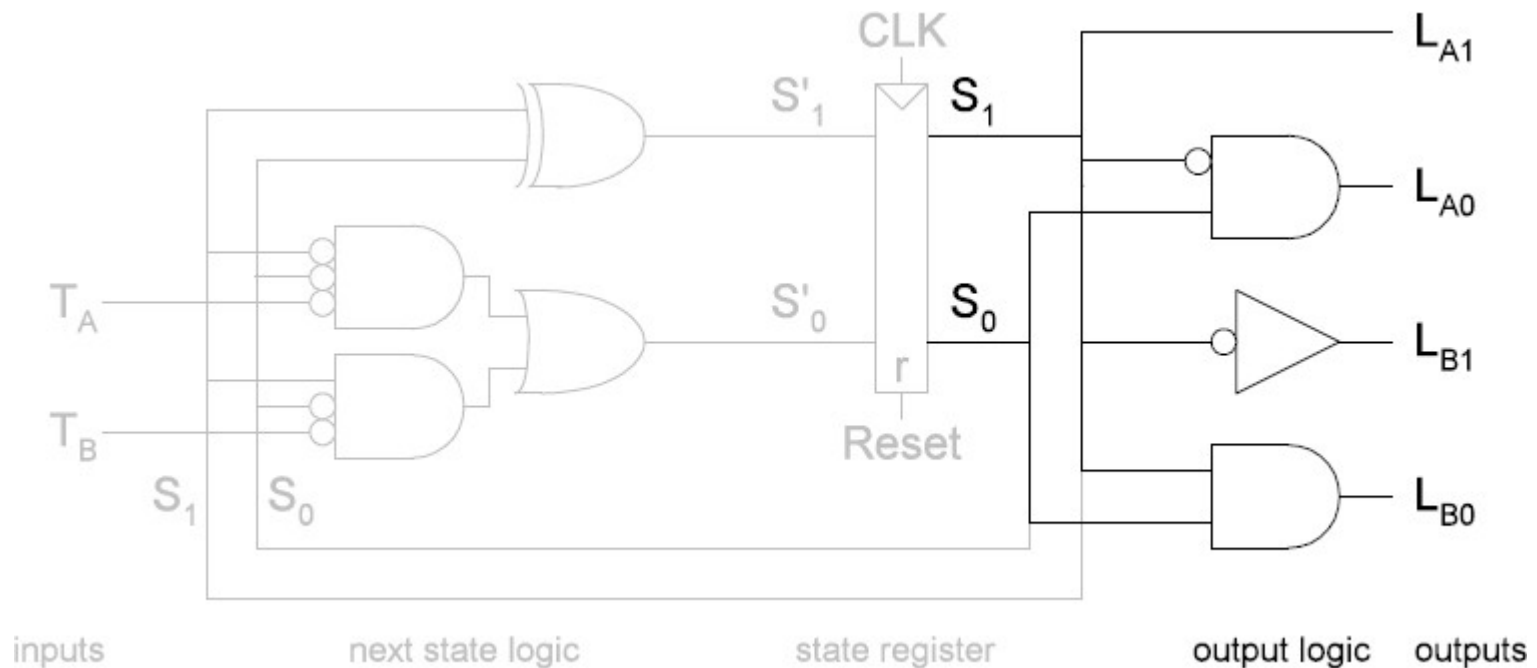

# FSM: divisible by 3

- Construct a "divisible by 3" FSM that accepts a binary number entered 1 bit at a time, MSB (most significant bit) first, and indicate with a light if the number entered so far is divisible by 3.

1)  $N \bmod 3$

$$0 \rightarrow N = 3p + 0$$

$$1 \rightarrow N = 3p + 1$$

$$2 \rightarrow N = 3p + 2$$

2) If the number so far is  $N$ , after a digit  $b$  is entered, the new number is  $N' = 2N + b$

$N \bmod 3$

$$0 \rightarrow N = 3p + 0, \text{ after digit } b \text{ is entered, } N' = 6p + b.$$

$$N' = b \bmod 3$$

$$1 \rightarrow N = 3p + 1, \text{ after digit } b \text{ is entered, } N' = 6p + 2 + b.$$


$$N' = b + 2 \bmod 3$$

$$2 \rightarrow N = 3p + 2, \text{ after digit } b \text{ is entered, } N' = 6p + 4 + b.$$

$$N' = b + 1 \bmod 3$$

# FSM: divisible by 3

## 1. State Transition Diagram

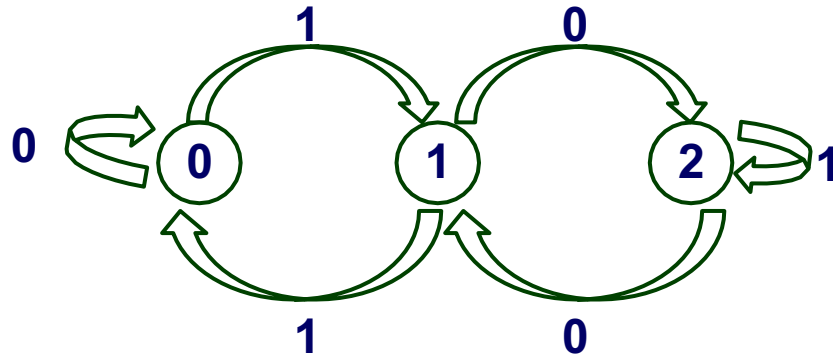

## 2. State Transition Table

S1	S0	b	S1'	S0'	light
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	1	0	0

## 2. State Encoding

State	S1	S0
0	0	0
1	0	1
2	1	0

## 3. Next State Logic

$$S1' = \overline{S1} \overline{S0} \overline{b} + S1 \overline{S0} b$$

$$S0' = \overline{S1} \overline{S0} b + S1 \overline{S0} \overline{b}$$

## 4. Output Logic

$$\text{light} = \overline{S1} \overline{S0}$$